
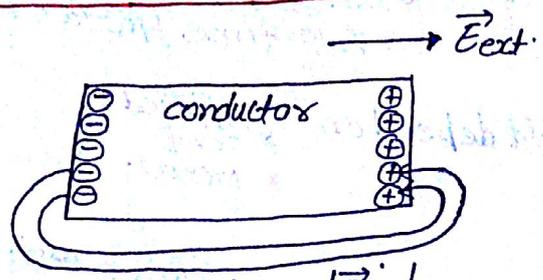


*** Electrodynamics

CURRENT ELECTRICITY

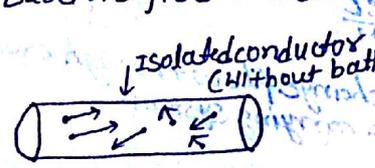

Electric field inside the conductor will be non-zero.



Due to thermal speed free e^- performed a random motion / brownian motion so net disp. of charge remain zero. So current is zero.

11) Free e^- density (n) → No. of free e^- in unit volume of metal ($n = 10^{28} e^-/m$).
* Depend on nature of metal. (Highest in silver).

12) Thermal speed (v_T) → Speed of free e^- due to surrounding temp.
K.E of one free e^-

$$\frac{1}{2} M v_T^2 = \frac{3}{2} kT$$

$$* v_T = \sqrt{\frac{3kT}{M}} \propto \sqrt{T}$$

* At room temp. $v_T = 10^5$ m/sec.

Ex → copper $n = 10^{29}/m^3$

$$u_{\text{thermal}} = 10^6 \text{ m/sec} = 1000 \text{ km/sec.}$$

* Net velocity of an e^-

$$\vec{v}_{\text{net}} = \vec{v}_{\text{thermal}} + \frac{e(-\vec{E})}{m} t$$

t = time b/w two successive collision.

$$* \langle \vec{v}_{\text{net}} \rangle = \langle \vec{v}_{\text{thermal}} \rangle + \left\langle \frac{e(-\vec{E})}{m} t \right\rangle$$


13) Relaxation time (τ) → It is average free time b/w two consecutive collision. $[\tau = 10^{-14} \text{ sec}]$ * also depend on metal.
 $1 \text{ sec} = 10^{14}$

AIR AIIMS

NOTE → ii) on ↑ temp. relaxation time ↓, hence drift speed ↓.
iii) Physical significance of Resistance -
The resistance offered by a conductor is due to collision of e^- with atoms of the lattice. So, on ↑ temp., resistance should also ↑.

14) Mean free path → (λ) → distance covering in τ (relative time)

$$\lambda = 10 \text{ \AA}$$

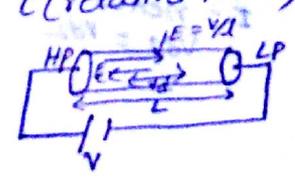

15) → Drift velocity (v_d) → After applying battery free e^- acquired almost velocity.

AIIMS
AIR

* Drift speed $\approx 10^{-3}$ m/sec / 10^{-4} m/sec / 0.1 mm/sec.
 10^{-3} m/sec, 10^{-2} cm/sec

$$\vec{v}_{drift} = -\frac{eE\tau}{m}$$

$$v_d = \left(\frac{e\tau}{m}\right)E$$

$$v_d = \left(\frac{e\tau}{m}\right)\left(\frac{V}{l}\right)$$

τ → Mean free time or, Relaxation time
or, Avg. time b/w two collision.

* v_d depend on → * Applied E
* Temp.
* Metal.

16) → Mobility (μ) → It is drift velocity for unit applied electric field.


$$E \rightarrow v_d$$

$$1 \rightarrow \frac{v_d}{E}$$

$$\mu = \frac{v_d}{E} = \frac{e\tau}{m}$$

17) → Electric current (I) → It is rate of change flow through cross sectional area of current carrying system.


$$I = \frac{dq}{dt}$$

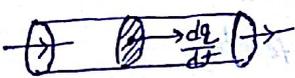

⇒ current → scalar quantity
* unit → M.K.S ⇒ C/sec, Amp.
C.G.S ⇒ Ab.Amp, Biot (Bi)

$$1 \text{ Ab.A} = 10 \text{ Amp}$$

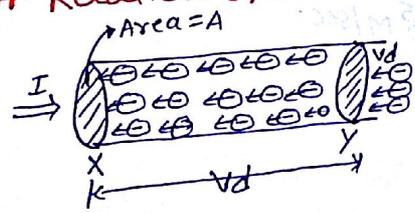
Relation b/w current (I) & drift speed (v_d) →



n = no. of free e^- per unit volume.
no. of e^- in volume $XY = n A v_d t$
charge crossing per sec = $A \times v_d \times n e = I$

$$I = n e A v_d$$

#

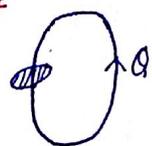

$$I = \frac{dq}{dt} = \frac{q}{T} = qf = \frac{qH}{2\pi} = \frac{qv}{2\pi r}$$

EX → calculate equivalent current in 1 orbit of H-atom.

$$I = \frac{ev}{2\pi r} = \frac{1.6 \times 10^{-19} \times 2.2 \times 10^6}{2 \times \pi \times 0.059 \times 10^{-10} \text{ m}} \approx 0.96 \text{ MA} \pm 1 \text{ MA}$$

* current carrying conductor always neutral.
 $E_{outside} = 0$, $E_{inside} \neq 0$ (due to battery)


* current at each point of conductor is same irrespective cross-sectional Area.



$$I_1 = I_2$$

$$I = n e A v_d$$

$$v_{d1} = v_{d2}$$

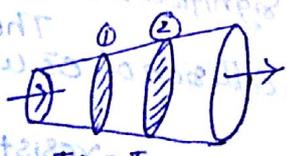

$$I_1 = I_2$$

$$I = n e A v_d$$



$$v_d \propto \frac{I}{A}$$

$$A_1 < A_2$$

$$v_{d1} > v_{d2}$$


* Area ka change v_d par
hota hai! I par nahi!

18) → current density (J) →

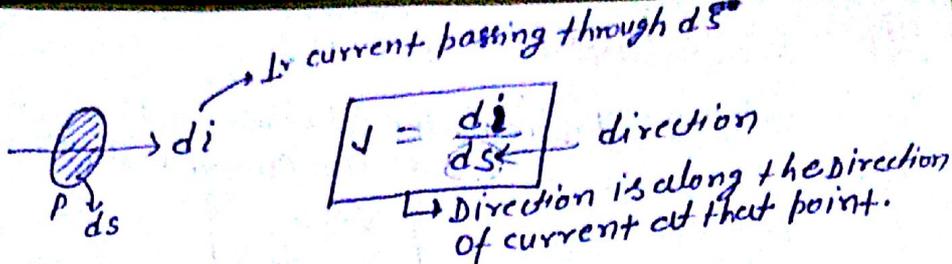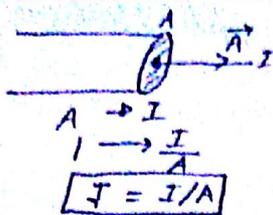

NOTE → ii) unit = $\frac{\text{Amp}}{\text{m}^2}$

iii) → If Area 'ds' is not ⊥

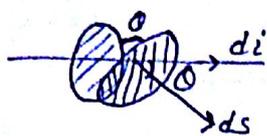

$$j = \frac{di}{ds \cos \theta}$$


$$* di = ds \cos \theta$$

$$\boxed{di = \vec{J} \cdot d\vec{s}}$$

$$i = \int di = \int \vec{J} \cdot d\vec{s}$$

$I = \oint \vec{J} \cdot d\vec{A}$ → current is flux of current density.] comparison.
 $Q = \oint \vec{E} \cdot d\vec{A}$ → charge is flux of electric density.]

In conductor →

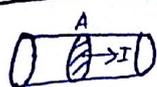

$$J = \frac{I}{A} = \frac{neAv_d}{A}$$

$$J = \frac{I}{A} = ne \left(\frac{eE}{m} \right) E$$

$$\boxed{J = \left(\frac{ne^2 \tau}{m} \right) E}$$

$$\boxed{J = \sigma E}$$

$$\boxed{\vec{J} = \sigma \vec{E}} \Rightarrow \text{vector form / microform of ohms law.}$$

19) → conductivity of specific conductance (σ) →

$$\sigma = \frac{ne^2 \tau}{m} = \frac{1}{\rho}$$

$$\text{Temp } \uparrow \propto \frac{1}{\tau} \propto \frac{1}{\sigma}$$

10) → Resistance (R) → tendency of current carrying system to oppose the charge flow.

$$V = IR, R = \frac{\text{Applied voltage}}{\text{Resultant current}}$$

* scalar
* unit → ohm (Ω)

Resistance of conductor →

$$I = neAv_d$$

$$= neA \left(\frac{eE}{m} \right) \tau E$$

$$\frac{V}{I} = \frac{m}{ne(e\tau)} \frac{l}{A}$$

$$\boxed{R = \left(\frac{m}{ne\tau} \right) \frac{l}{A}}$$

$$R = \frac{\rho l}{A}$$

(2) (3) (4) (5) (6) (7) (8) (9) (10) (11) (12) (13) (14) (15) (16) (17) (18) (19) (20) (21) (22) (23) (24) (25) (26) (27) (28) (29) (30) (31) (32) (33) (34) (35) (36) (37) (38) (39) (40) (41) (42) (43) (44) (45) (46) (47) (48) (49) (50) (51) (52) (53) (54) (55) (56) (57) (58) (59) (60) (61) (62) (63) (64) (65) (66) (67) (68) (69) (70) (71) (72) (73) (74) (75) (76) (77) (78) (79) (80) (81) (82) (83) (84) (85) (86) (87) (88) (89) (90) (91) (92) (93) (94) (95) (96) (97) (98) (99) (100)

11) → Resistivity or, Sp. Resistance (ρ) →

$$\rho = \frac{m}{ne^2 \tau} = \frac{1}{\sigma}$$

* unit = Ω·m
* temp ↑, τ ↑, ρ ↓

AIPMT 2002

* Resistance depend on length/Area but Resistivity (ρ) doesn't depend on this both parameter.

Ohm's Law

In conductor at const temp. current is \propto applied voltage so, resistance remain const.

$$\left[\begin{array}{l} V \propto I \\ \frac{V}{I} = \text{const} \\ R = \text{const} \end{array} \right] \rightarrow \text{means ohm's voltage.}$$

$$I = A V_d n e$$

$$\frac{I}{A} = V_d n e = \frac{e^2 n E \tau}{m}$$

$$* \vec{J} = \frac{e^2 n \vec{E} \tau}{m}$$

$$* \frac{|\vec{E}|}{|\vec{J}|} = \frac{m}{e^2 \tau n} = \rho (\text{Resistivity})$$


lit* $\rightarrow \rho$ is a property of material. (इसका कोई तार नहीं जिसका कोई R नहीं है!)
 AIEEE III \rightarrow on \uparrow temp.

AMU 2016/1* \rightarrow For conductor \uparrow as τ decreases.
 For semiconductor \downarrow
 $\rightarrow \tau \downarrow$
 $\rightarrow n \uparrow$
 $\rightarrow n\tau \uparrow$ se.

$$\text{iiit} \rightarrow \rho_T = \rho_0 (1 + \alpha \Delta T)$$

α = Temp. coefficient of resistivity.
 ΔT = Rise in temp.

iv \rightarrow special case

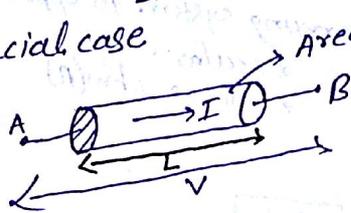

$$\begin{array}{l} E = \frac{V}{L} \\ J = \frac{I}{A} \\ \frac{E}{J} = \frac{m}{e^2 \tau n} = \rho \end{array} \left| \begin{array}{l} \frac{V}{I} = \rho \frac{L}{A} \\ \frac{V}{I} = R (\text{Resistance}) \end{array} \right.$$

* Resistance depends on material as well as physical dimensions.

$$* \text{conductivity } (\sigma) = \frac{1}{\text{resistivity } (\rho)}$$

$$* \text{conductance} = \frac{1}{\text{Resistance } (R)}$$

* unit -

Resistance \rightarrow ohm (Ω)

Resistivity \rightarrow ohm-meter

conductivity \rightarrow mho- m^{-1}
 conductance \rightarrow mho or Siemen.

Dependence of conductor Resistance \rightarrow

$$\text{AIPMT} \quad R = \frac{\rho l}{A} \times \frac{l}{J}$$

$$R = \frac{312}{\text{vol}}$$

~~Area~~
Length (l) →

ii) → If $A = \text{const} \Rightarrow R = \frac{\rho l}{A} \Rightarrow R \propto l$

iii) → If $\text{vol} = \text{const} \Rightarrow R = \frac{\rho l^2}{\text{vol}} = R \propto l^2$

Cross Section Area (A) →

ii) → If $l = \text{const} \Rightarrow R = \frac{\rho l}{A} \Rightarrow R \propto \frac{1}{A} \propto \frac{1}{r^2}$

iii) → If $\text{vol} = \text{const} \Rightarrow R = \frac{\rho(\text{vol})}{A^2} \Rightarrow R \propto \frac{1}{A^2} \propto \frac{1}{r^4}$

iiii) → Temp.

lv) → Metal.

*** Stretching, compressing, melting, moulding, Bending means $\text{vol} = \text{const.}$**

EX → Resistance of conducting wire is 'R' calculate Resistance if -

ii) → Its length become 'n' times by stretching it -
 $\Rightarrow l' = nl$ (vol. const), $R \propto l^2$, $R' = n^2 R$

iii) → If radius become $\frac{r}{n}$ times by stretching it -
 $r' = r/n$
 $\text{vol} = \text{const}$ (beoz wire stretched)

$R \propto \frac{1}{r^4}$, $R' = n^4 R$

iiii) → If wire is folded into 'n' layers.
 $\text{vol} = \text{const.}$

$l' = l/n$
 $R \propto l^2$ | $R' = \frac{R}{n^2}$

Imp # Small % change at const vol:

ii) → If $\Delta l = x\%$ then $\Delta R = 2x\%$

iii) → If $\Delta A = x\%$ then $\Delta R = -2x\%$

iiii) → If $\Delta r = x\%$ then $\Delta R = -4x\%$

*** Trick**

$$R \propto l^2$$

$$R \propto \frac{1}{A^2} \propto A^{-2}$$

$$R \propto \frac{1}{r^4} \propto r^{-4}$$

EX → * stretching a wire l 2% ↑
 R 4% ↑

* By compressing a metal block cross section area by 1% → $R = 2\% \downarrow$

EX → $P = I^2 R$

If $\Delta I = x\% \Rightarrow \Delta P = 2x\%$

ii) → If $I \rightarrow 1\% \downarrow$
 $P \rightarrow 2\% \downarrow$

iii) → If $I_{\text{bulb}} = 0.5\% \downarrow$
 $P \rightarrow 1\% \downarrow$

EX → $r \rightarrow 1\% \uparrow$
 $F = \frac{kq_1 q_2}{r^2}$

$f = r^{-2}$
 $F = -2x = -2\% \downarrow$

Dependence of Resistance on temp. →

In conductor

Temp ↑ ⇒ $\rho \downarrow \Rightarrow P \uparrow \Rightarrow \text{Resistance} \uparrow$

⇒ Resistance temp. const. (α)

i) $\alpha = \frac{\Delta R/R}{\Delta t}$

ii) unit \rightarrow per unit temp.
per °C
per K

iii) \rightarrow If α (high) = more variation in Resistance.
If α (low) = less))))))

iv) \rightarrow If α (+ve) \Rightarrow Temp $\uparrow \Rightarrow R \uparrow \Rightarrow$ Metal.
If α (-ve) \Rightarrow Temp $\uparrow \Rightarrow R \downarrow \Rightarrow$ semiconductor.
If $\alpha = \text{zero} \Rightarrow$ Temp $\downarrow \Rightarrow R = \text{const} \Rightarrow$ Insulator.

v) $\rightarrow R_{t2} = R_{t1} [1 + \alpha (t_2 - t_1)]$

If Reference temp. = 0°C

$R_t = R_0 [1 + \alpha (t)]$

Take care \rightarrow Temp. should be in °C
This relation valid for small temp. change.
Reference temp. taken in 0°C or 20°C

Imp
##


If series Resistance is independent of temp. then $\alpha = 0$

$$\alpha_{\text{series}} = 0 \quad \left| \quad R_1 \alpha_1 = -R_2 \alpha_2 \right.$$

$$0 = \frac{R_1 \alpha_1 + R_2 \alpha_2}{R_1 + R_2} \quad \left| \quad \frac{R_1}{R_2} = -\frac{\alpha_2}{\alpha_1} \right.$$


* This condition one wire should be conductor other should be semiconductor.

Graph: \rightarrow Resistance v/s temp.

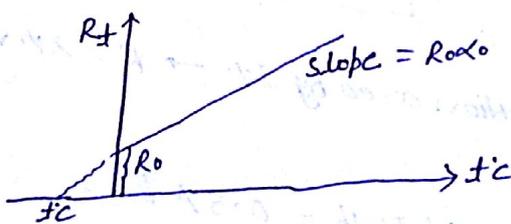

$R_t = R_0 (1 + \alpha_0 t)$
 $R_t = R_0 t (R_0 \alpha_0) t$

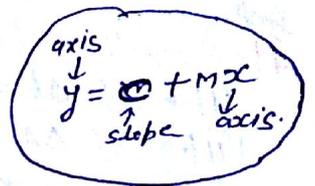* $\left[\begin{array}{l} \text{If } t > t_c \Rightarrow R \neq 0 = \text{conductor} \\ \text{If } t \leq t_c \Rightarrow R = 0 = \text{superconductor} \end{array} \right.$



Some special materials: -

i) Heating element \rightarrow * High MP, High resistivity
* Nichrome
* $S_{\text{alloy}} > S_{\text{metal}}$

ii) Standard Resistance \rightarrow * Small (α)
* Alloy $<$ metal

* Best alloy is magnenium, constantum, evertung.


**

iii) Fused wire \rightarrow * It is used to protect the ckt from excess current.
Imp Always connected in series at the starting of ckt.

* MP small
* Made of Sn + Pb
63% 37%
* current capacity (I)
 $I \propto r^{-3/2}, I \propto d^0$

CIRCUIT

1.1 → Grouping of Resistance →

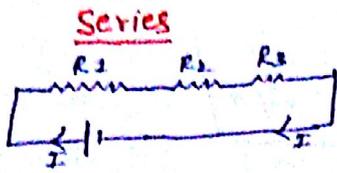

- * current \Rightarrow same
- * $R_{net} = R_1 + R_2 + R_3$
- * $R_2 > R_1$
- $R_2 > R_2$
- $R_2 > R_3$


* voltage distribution

$$V = IR$$

Same

$$V \propto R$$

$$V_1 : V_2 : V_3 = R_1 : R_2 : R_3$$

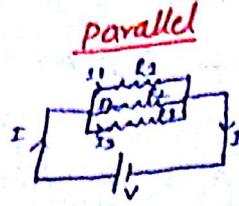

- * current \Rightarrow different in ||
- * $V =$ same
- * $\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$
- $R_{eq} = \frac{R_1 R_2}{R_1 + R_2}$
- $R_{eq} < R_1$
- $R_{eq} < R_2$
- $R_{eq} < R_3$

* current distribution


$$V = IR$$

$$I = \frac{V}{R}$$

$$I_1 : I_2 : I_3 = \frac{1}{R_1} : \frac{1}{R_2} : \frac{1}{R_3}$$


* **LOWIC** \Rightarrow जिसमें Resistance कम उसमें voltage कम !

IIT
EX \rightarrow

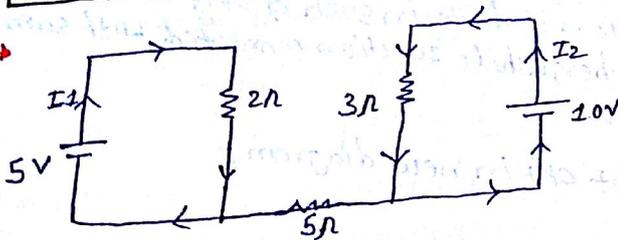

$I_{5\Omega} = ? = 2\text{A}$
* current अपना रास्ता repeat नहीं करता !!

EX \rightarrow

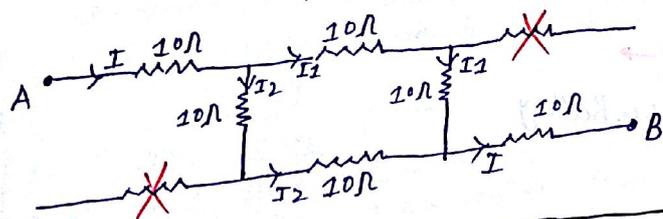

$$R_{AB} = 10 + 10 + 10 = 30\Omega$$

* current का flow उसी direction में जैसा जो जाता है जिसमें wo अपना आरंभिक संकीर्ण तक पहुँचता है!


Short trick \rightarrow consider 1st two block only get their Resistance after that
 ii) $R_{eq} \leq R_{approx}$ [R = Resistance] [R for Resistance, R for Reduce]
 iii) $C_{eq} \geq C_{approx}$ [C = capacitor]



$$* R_{eq} = r + \frac{3r}{4} + r = \frac{11r}{4} = 2.75r$$

* R_{eq} is slightly less than $2.75r$

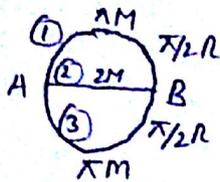EX → Find equivalent Resistance of given ckt Made up of conducting wire.



radius = 2M

Resistance = $\frac{1}{2} \Omega/M$

circumference of circle ($2\pi M$) = 2π → ① = π
→ ③ = π

$$R_{AB} = \frac{2}{\pi} + \frac{2}{\pi} + 1$$

$$= \frac{4 + \pi}{\pi}$$

$$\frac{1}{R_{AB}} = \frac{4 + \pi}{\pi}$$



$$R_{AB} = \frac{\pi}{\pi + 4}$$

Current जयवा रररर Repeat रररर रररर!

short circuit →

ii) → $R = 0$ path

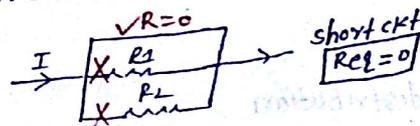
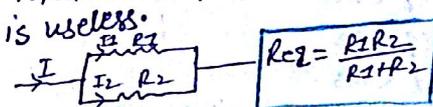
iii) → Total current passed through ckt path so component passes through short ckt path is useless.



open circuit →

ii) → $R = \infty$

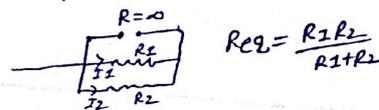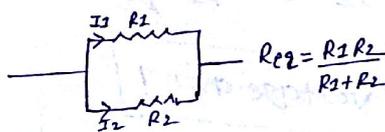iii) → In this case current is zero, bcoz problem is a resistance.




point potential method → It is useful in ckt having direct wires (component free path).


ii) → Numbering of all junction is done in such a way that different junction should have number, while junction connected with same wire have same number.

iii) → Rearrange the component ckt in new diagram.

Battery With Internal Resistance →

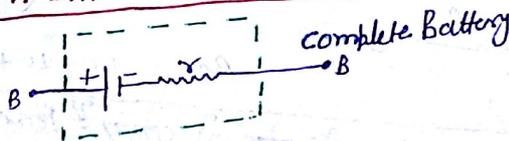


* During Discharging

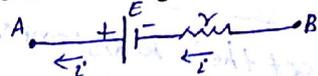


$$V_A - V_B = +E - ir < \text{Emf of Battery}$$

* During charging

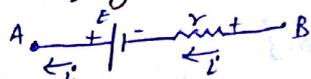

$$V_A - V_B = +E - ir > \text{Emf of Battery}$$

* When open ckt

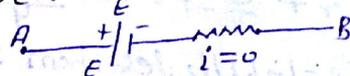

$$V_A - V_B = +E = \text{Emf of battery}$$


NOTE →

ii) → Power supplied/consumed by Battery.



* Work done by battery in time 'dt' = (dq)E = dw
 * Rate of Work done ($\frac{dw}{dt}$) = $E \frac{dq}{dt} = Ei = P_{supplied}$.
 * During charging $P_{consumed} = Ei$

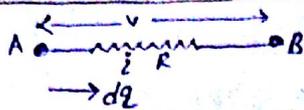iii) → Heat lost in a Resistance : → (Joule Heating).



If 'dq' charge passes through 'R' from 'A' to 'B'
 Energy lost by (dq) :

$$P_{loss} = \frac{dH}{dt} = V \cdot \frac{dq}{dt} = Vi$$

$$P_{loss} = Vi = i^2 R = \frac{V^2}{R}$$

Heat los in time 't'

$$H = Pt = i^2 R t$$

$$P = H/t$$

Kirchoff LAW

- KCL
- KVL

ii) → First law/current law/Junction law (KCL) : →

→ Based on charge conservation.

→ At any junction algebraic sum of all current or charges is always zero.
 It means current towards junction is exactly equal to current leaving the junction.

$$\Rightarrow \sum Q = 0 \quad | \quad \Rightarrow \sum I = 0 \quad | \quad \Rightarrow I_{incoming} = \text{Ove while outgoing } \text{Ove.}$$

iii) → second law/voltage law/Loop law (KVL) : →

→ Based on Energy conservation.

→ In a close loop summation of all p.d is always zero.

$$\sum PD = 0$$

* # Sign conversion →

observer →	⊙	⊙ to ⊙ → ⊖ve	vi →	- + → +V	
	⊙	⊙ to ⊕ve → ⊕ve		vii →	$\frac{+}{I} \frac{+}{R} \rightarrow -IR$
	⊙	⊙ to ⊕ve → ⊕ve		viii →	$\frac{-}{R} \frac{+}{I} \rightarrow +IR$
	⊙	⊙ to ⊕ve → ⊕ve			
	⊙	⊙ to ⊕ve → ⊕ve			
	⊙	⊙ to ⊕ve → ⊕ve			
	⊙	⊙ to ⊕ve → ⊕ve			
	⊙	⊙ to ⊕ve → ⊕ve			
	⊙	⊙ to ⊕ve → ⊕ve			


Symmetrical line method : →

- Draw the ⊥ bisector line joining the terminals points. This symmetrical line should draw the ckt in two mirror image.
- stretch the ckt along symmetrical line in such way that all function on symmetrical line are removed.

Circuit Based on Wheat stone Bridge →


Case-I → Balance Bridge →
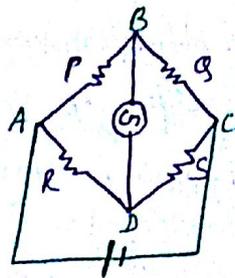
$$\text{If } \frac{P}{Q} = \frac{R}{S} \quad \begin{cases} V_B = V_D \\ I_{\text{middle}} = 0 \end{cases}$$



AIIMS

EX →

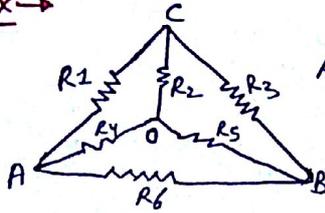

All Resistance same value = ?

If Battery Applied that B/w

$$\begin{array}{l|l} A \neq O \Rightarrow I_{R3} = 0 & A \neq B \Rightarrow I_{R2} = 0 \\ B \neq O \Rightarrow I_{R1} = 0 & B \neq C \Rightarrow I_{R4} = 0 \\ C \neq O \Rightarrow I_{R6} = 0 & A \neq C \Rightarrow I_{R5} = 0 \end{array}$$

Case-II → Unbalance Bridge →

$$\text{If } \frac{P}{Q} \neq \frac{R}{S} \quad V_B \neq V_D \Rightarrow I_{\text{middle}} \neq 0$$

* If $\frac{P}{Q} > \frac{R}{S} \Rightarrow V_B < V_D$

Battery side also same A/c to diagram.


* If $\frac{P}{Q} < \frac{R}{S} \Rightarrow V_B > V_D$

* For gating equivalent Resistance KVL & star delta method used.

* short circuit → If unbalanced bridge is also eliminated the middle arm & get resultant which is approx.

$$\begin{array}{l} \text{ii) } \rightarrow R_{eq} \leq R_{\text{approx}} \\ \text{iii) } \rightarrow C_{eq} \geq C_{\text{approx}} \end{array}$$

*** # Star - delta method.

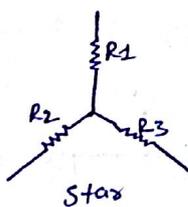

* Star to Delta →

$$\begin{array}{l} R_{12} = R_1 + R_2 + \frac{R_1 R_2}{R_3} \\ R_{13} = R_1 + R_3 + \frac{R_1 R_3}{R_2} \\ R_{23} = R_2 + R_3 + \frac{R_2 R_3}{R_1} \end{array}$$


* Delta to Star →

$$\begin{array}{l} R_1 = \frac{R_{12} R_{13}}{(R_{12} + R_{23} + R_{13})} \\ R_2 = \frac{R_{12} + R_{23}}{(R_{12} + R_{23} + R_{13})} \\ R_3 = \frac{R_{23} R_{13}}{(R_{12} + R_{23} + R_{13})} \end{array}$$

NOTE → About Wheat stone Bridge -

- * Battery arm & galvanometer are interchangeable.
- * Battery key (K1) is made on first then galvanometer key is opened to avoid the effect of induced current.
- * Battery is most sensitive. When all four Resistance are of same value.

cube

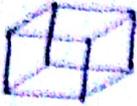

Each side = Resistance (R)

- * Face diagonal = $\frac{5}{4}R = 0.82$
- * Space diagonal = $\frac{7}{4}R = 0.75$
- * R side = $\frac{3}{4}R = 0.58$

Each side = capacitance (C)

- * Capacitance div = $\frac{6}{5}C$
- * C face div = $\frac{4}{3}C$
- * C side = $\frac{12}{7}C$

CELL

chemical energy into electrical energy.

- * Pri-cell → non-rechargeable, chemical rxn irreversible, High 'v'.
- * Sec-cell → Rechargeable, chemical rxn reversible, Low 'v'.

$\frac{r}{R+r}$
 r = internal resistance of cell
 * Practically $r \neq 0$
 * ideally $r = 0$

EMF of cell (E)

- * It is work done by cell in a rotating unit charge in complete circle.
- * It is PD b/w cell terminal when current with cell is zero.
- * All pointed or mentioned values are EMF only.

Terminal voltage (V)

|1| → It is PD b/w cell terminal when current with cell is non-zero.

$$V = E - IR \quad [\text{Discharging } \leftarrow | -]$$


$$V = E + IR \quad [\text{charge } \rightarrow | -]$$

|2| → cell is open ckt.

$$R = \infty \quad I = 0 \quad \boxed{V = E}$$

NOTE → Terminal voltage may be more, less or equal to emf.

cell ckt →

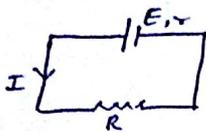

|i| → $I_{ckt} = \frac{E}{R+r}$

|ii| → $I_{max} = \frac{E}{r}$ [When Load Resistance 'R' = 0]

|iii| → $V = E - IR$

|iv| → $r = \left(\frac{E-V}{I}\right) R$

- |v| → Power at Load (P) = $I^2 R$
 * Power in ckt (P) = $I^2 (R+r)$
 * $P_{load} = I^2 R = \left(\frac{E}{R+r}\right)^2 R$


|vi| → $P_{max} \frac{dP}{dR} = 0 \quad \boxed{R = r}$

$P_{max} = \frac{E^2}{4R}$

NOTE → * $r = 0$ then $I_{max} = \frac{E}{r}$
 * $R = r$ then $P_{max} = \frac{E^2}{4R}$

Grouping of cell

|1| → Series →

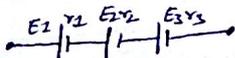

$$E_{net} = E_1 + E_2 + E_3$$

$$r_{net} = r_1 + r_2 + r_3$$

Case-I → If $R \ll nr \rightarrow I = \frac{nE}{nr} = \frac{E}{r}$

Case-II → $R \gg nr \rightarrow I = \frac{nE}{R} = n \left(\frac{E}{R}\right)$

Imp * If one battery, say E_3 is connected with terminals is reversed.


$$E_{equi} = E_1 + E_2 - E_3$$

$$r_{equi} = r_1 + r_2 + r_3$$

* If n-Batteries each having different emf & their emf are proportional to their internal resistance i.e. $E \propto r$

NOTE → If Load Resistance (R) is very-very large than total internal resistance then series grouping of cell is preferred.

12) → Parallel →

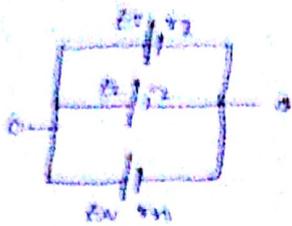

$$E_{net} = \frac{E_1}{\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3}}$$

$$r_{net} = \frac{1}{\frac{1}{r_1} + \frac{1}{r_2} + \frac{1}{r_3}}$$


r_{net} = || equivalent of all 'r'



$$E_{net} = \frac{E_1 r_2 + E_2 r_1}{r_1 + r_2}$$

$$r_{net} = \frac{r_1 r_2}{r_1 + r_2}$$

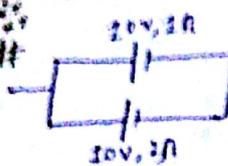NOTE → Here E_{net} is b/w E_1 & E_2 only in this case.



$$E_{net} = \frac{20 + 10}{3} = \frac{30}{3} = 10V$$

* → If || cell in same polarity →


- ii) → E_{net} b/w E_1 & E_2 .
- iii) → If EMF of each cell is same then E_{net} is equal to EMF of one cell.

Case-I → If $R \gg \frac{r}{n} \Rightarrow I = E/R$
Case-II → If $\frac{r}{n} \gg R \Rightarrow I = nE/r$

* If $E_1 = E_2 = E_3 = E$
 $r_1 = r_2 = r_3 = r$
 $E_{eq} = E$
 $r_{eq} = r/3$

Symmetrical mixed grouping →

'n' identical cell (E, r) →

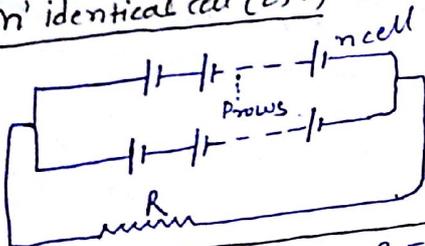

$$I = \frac{nE}{R + \frac{nr}{p}}$$

* For $P_{max} = R = \frac{nr}{p}$

$$\frac{R}{r} = \frac{n}{p}$$

* $I_{max} = \frac{R}{r} = \frac{n}{p}$

n-identical resist.

$$H = \frac{V^2}{R} \propto \frac{1}{R}$$



$$\frac{H_{series}}{H_{parallel}} = \frac{R_{parallel}}{R_{series}} = \frac{R/n}{nr} = \frac{1}{n^2}$$

* Temp. change $H = ms\Delta\theta$ * Phase change $H = ML$
 * $S_{water} = 1 \text{ cal/gm}^\circ C$ * $L_{ice} = 80 \text{ cal/gm}$ * $L_{water} = 540 \text{ cal/gm}$

BULB



→ Rated values (V_R & P_R) →

EX → Bulb (100W, 220V)

$$V_R = 220V$$

$$P_R = 100W$$

- * If $V_{actual} = 220V$, $P_{actual} = 100W \Rightarrow$ Perfect.
- * If $V_{actual} < 220V$, $P_{actual} < 100W \Rightarrow$ Dim
- * If $V_{actual} > 220V$, → Fused.

* Resistance of Bulb (R_B) This is always calculated using Rated value only.

$$R_B = \frac{V_R^2}{P_R}$$

(ii) → In India ($V_R = \text{same}$)

$$R_B \propto \frac{1}{P_R}$$

EX → $R_{100W} < R_{60W} < R_{40W}$

* Actual power consumption of Bulb →

$$P_{actual} = I_{actual}^2 R_B = \frac{V_{actual}^2}{R_B}$$

Brightness \propto Pactual

Case-I → Bulb in series →

Brightness \propto Pactual ($= I^2 R_B$)

$$\propto R_B$$

$$\propto \frac{1}{P_R}$$

- NOTE →
- * In series bulb of less rated power is more bright.
 - * Bulb with higher Poutput will glow more.
 - * Bulb with higher Resistance will glow more.

Case-II → Bulb in Parallel →

Brightness \propto Pactual ($\frac{V^2}{R_B}$)

$$\propto \frac{1}{R_B}$$

$$\propto P_R$$

- NOTE →
- * Bulb of less rated power is less bright.
 - * Bulb with lower Resistance will glow more.

#

$$P_{total} = \sum P(\text{parallel})$$

$$P_{total} = \sum \frac{1}{P}(\text{series})$$